## **Choosing the Right Memory IC:**

o For Small Non-Volatile Data Storage:

**EEPROM**: AT24C256 (256 Kbit), easy to interface with I2C.

For Larger Non-Volatile Storage:

Flash Memory: W25Q64 (64 Mbit), interfaced using SPI.

For Large Volatile Storage:

**SRAM**: 23LC1024 (1 Mbit), interfaced using SPI.

o For *Very Large Storage* Needs:

**SD Card Module**: Supports up to several gigabytes, interfaced using SPI.

## **Hardware Requirements and Connections:**

### 1. External EEPROM (AT24C256)

## **Components:**

AT24C256 EEPROM

AT24C256 Robu.com 256 Kbit (No 1 Mbit option available)

Arduino Uno

Pull-up resistors (typically  $10k\Omega$ )

Connecting wires

**Breadboard** 

### Wiring:

SDA (EEPROM) -> A4 (Arduino)

SCL (EEPROM) -> A5 (Arduino)

VCC (EEPROM) -> 5V (Arduino)

GND (EEPROM) -> GND (Arduino)

WP (EEPROM) -> GND (Arduino)

Pull-up resistors between SDA and VCC, and SCL and VCC

# 2. External Flash Memory (W25Q64)

### **Components:**

```
W25Q64 Flash Memory
```

WQ25 RoboCraze.com Module 64 Mbit

Flash Module Robu Buy link (W25Q128 8Mbit)

Arduino Uno

Pull-up resistors (typically  $10k\Omega$  for CS, optional for other SPI lines)

Connecting wires

**Breadboard** 

#### Wiring:

```
MISO (Flash) -> 12 (Arduino)
```

MOSI (Flash) -> 11 (Arduino)

SCK (Flash) -> 13 (Arduino)

CS (Flash) -> 10 (Arduino)

VCC (Flash) -> 3.3V (Arduino)

GND (Flash) -> GND (Arduino)

### 3. External SRAM (23LC1024)

#### **Components:**

23LC1024 SRAM

23LC1024 1 Mbit Arrow Price

Arduino Uno

Pull-up resistors

Connecting wires

Breadboard

#### Wiring:

MISO (SRAM) -> 12 (Arduino)

MOSI (SRAM) -> 11 (Arduino)

```
SCK (SRAM) -> 13 (Arduino)
```

CS (SRAM) -> 10 (Arduino)

VCC (SRAM) -> 5V (Arduino)

GND (SRAM) -> GND (Arduino)

# 4. SD Card Module

### **Components:**

SD Card Module

UNO Rev3 with built in SD Card Module

MicroSD Card

Arduino Uno

Connecting wires

Breadboard

### Wiring:

MISO (SD Module) -> 12 (Arduino)

MOSI (SD Module) -> 11 (Arduino)

SCK (SD Module) -> 13 (Arduino)

CS (SD Module) -> 10 (Arduino)

VCC (SD Module) -> 5V (Arduino)

GND (SD Module) -> GND (Arduino)

## **Comparison:**

Price: Flash < EEPROM < SRAM < SD Card Module

Storage availability: SD Card Module> (Flash = SRAM)> EEPROM

Memory Type	Interface	Max Clock Speed	Write Speed	Read Speed	Use Case
AT24C256 EEPROM	I2C	400 kHz	~5 ms per byte	Limited by I2C speed	Small non-volatile storage, speed not critical
W25Q64 Flash	SPI	104 MHz (quad)	Page program ~1.5 ms	Up to 50 MB/s (quad)	Large non-volatile storage, faster read/write
23LC1024 SRAM	SPI	20 MHz	Instantaneous	Instantaneous	Large volatile storage, very fast
SD Card Module	SPI	25 MHz (typical)	2-20 MB/s	20-90 MB/s	Very large storage needs, moderate read/write speed

So, considering these parameters we can conclude that flash memory will be the best option as external memory.